

```

module m4_1e_testbench();
    reg input3;
    reg [3:0] input_bus;
    reg [1:0] input_bus2;
    wire output1;
    //wire [3:0] output_bus1;

    m4_1e    UUT    ( .in(input_bus), .sel(input_bus2), .e(input3),
                     .o(output1));

// below is the "stimuli," the values for the inputs
// be sure to select a range of inputs that will fully exercise your design

    initial
    begin

        //----- Current Time:  0ns
        //input1=1'b0;
        //input2=1'b0;
        input3=1'b1;
        input_bus = 4'b0000;
        input_bus2 = 2'b00;
        #100; //This advances time by 100 units (ns in this case)
        // ----- Current Time:  100ns
        input_bus = 4'b1100;
        input_bus2 = 2'b00;
        #100; // ----- Current Time:  200ns
        input_bus2 = 2'b01;
        #100; // ----- Current Time:  300ns
        input_bus2 = 2'b10;
        #100; // ----- Current Time:  400ns
        input_bus2 = 2'b11;
        #100; // ----- Current Time:  500ns
        input_bus = 4'b1111;
        input_bus2 = 2'b00;
        #100; // ----- Current Time:  600ns
        input_bus2 = 2'b01;
        #100; // ----- Current Time:  700ns
        input_bus2 = 2'b10;
        #100; // ----- Current Time:  800ns
        input_bus2 = 2'b11;
        #100; // ----- Current Time:  900ns
        input3=1'b0;

    end
endmodule

```